

Assigment 4

Muthya Narayanachary Akhil (A0229794L)

February 12, 2024

Question 1

$A_k = 1$ and $B_k = 1$ for all $k = 0 \dots N-1$

Question 2

Part a

We know that the delay of an N-bit adder with M-bits per stage is:

$$t_{add} = t_{setup} + M * t_{carry} + \frac{N}{M} * t_{mux} + t_{sum} \quad (1)$$

This means that:

$$t_{add} = 2 + M + \frac{32}{M} + 2 = 4 + M + \frac{32}{M} \quad (2)$$

We know that the delay for an N-bit ripple carry adder is:

$$t_{add,ripple-carry} = (N - 1)t_{carry} + t_{sum} = 33 \quad (3)$$

Based on equations (2) and (3) we can claim that if $M \geq 3$, the carry select adder has less propagation delay than the ripple-carry adder.

Part b

Based on the equations (1) and (3) we can claim:

$$T_{add,select-carry} = 2 + 4 * 1 + \frac{N}{2} * 1 + 2 = \frac{N}{2} + 8 \quad (4)$$

$$T_{add,ripple-carry} = (N - 1) * 1 + 2 = N + 1 \quad (5)$$

We assumed that $T_{add,select-carry} < T_{add,ripple-carry}$, that is

$$\frac{N}{2} + 8 \leq N + 1 \quad (6)$$

$$N + 16 \leq 2N + 2 \quad (7)$$

That is $N \geq 14$. Hence if $N \geq 14$ then the carry select adder has lesser propagation delay.