

# Assigment 5

Muthya Narayanachary Akhil

February 19th, 2024

## Question 1

### Part a

When  $Q = 1$  and  $\overline{Q} = 0$  and  $WL = H$ , this implies that M5 and M1 form a voltage ladder. Hence the  $\overline{Q}$  is deduced by this equation:

$$\overline{Q} = V_{DD} * \frac{R_{M1}}{R_{M5} + R_{M1}} \quad (1)$$

Hence we can observe the following:

$$1 * \frac{R_{M1}}{R_{M5} + R_{M1}} < 0.4. \quad (2)$$

$$6 * R_{M1} < 4 * R_{M5} = R_{M1} < \frac{2}{3} * R_{M5} \quad (3)$$

This implies that  $W_{M1}$  should be greater than  $1.5 \mu m$ .

### Part b

When  $Q = 1$  and  $\overline{Q}=0$ , M2 and M3 are off, so the writing part is done by M4 and M6 instead. M4 and M6 form a voltage ladder, hence voltage at this point can be given to be:

$$1 * \frac{R_{M6}}{R_{M4} + R_{M6}} < 0.4 \quad (4)$$

$$6 * R_{M6} < 4 * R_{M4} \quad (5)$$

That is,  $W_{M4}$  must be less than  $\frac{2}{3} \mu m$ .

## Question 2

### Part a

As we know,

$$Q_{overall} = Q_{BL(initial)} + Q_{S(initial)} \quad (6)$$

Based on the data we already know, we can infer the following:

$$(80fF + 20fF) * V_{final} = 80tF * 1 \quad (7)$$

$$V_{final} = 0.8V \quad (8)$$

Hence the dropping amount is  $1 - 0.8 \text{ V} = 0.2 \text{ V}$

### **Part b**

This results in a potential drop from M1. The top plate of  $C_s$  can only reach 1.6 V. To prevent such a voltage drop, M1's gate voltage needs to have  $V_{th,M1}$  higher than BL. This would minimally need to be 2.4 V or higher, this process is commonly called bootstrapping.