

Assigment 3

Muthya Narayanachary Akhil

February 5, 2024

Question 1


Part a

Based on the lecture notes, the boolean expression can be calculated to be the following:

$$OUT = (A + B) \cdot (C \cdot D + E) \quad (1)$$

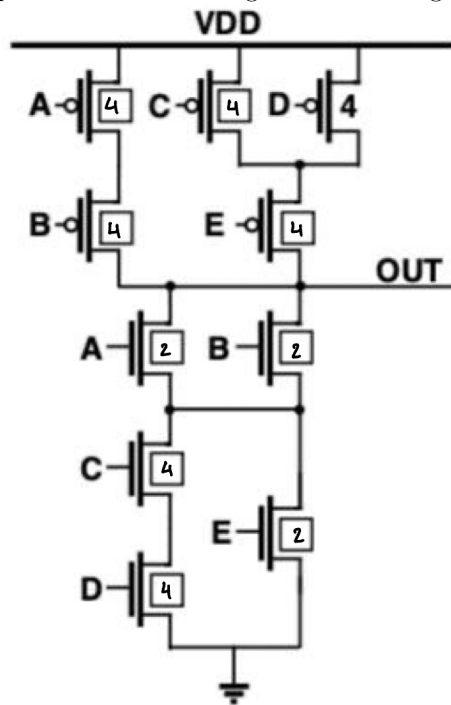Part b

The appropriate transistor sizing is the following:



Part c

As discussed in the lecture, the output is low and R_{out} is at its lowest when all the inputs are high That is:

$$A = 1, B = 1, C = 1, D = 1, E = 1, \quad (2)$$

This resistance value is equal to:

$$R_{out} = \frac{\frac{12k}{2}}{\frac{12k}{2}} + \frac{\frac{12k}{4} + \frac{12k}{4}}{\frac{12k}{2}} = 6k\Omega \quad (3)$$

Part d

Similarly, when the output is high, R_{out} is lowest when all the inputs are low. That is:

$$A = 0, B = 0, C = 0, D = 0, E = 0 \quad (4)$$

And the output resistance can be calculated to be:

$$R_{out} = \frac{\frac{12k}{2} + \frac{12k}{2}}{\frac{\frac{12k}{2}}{2} + \frac{12k}{2}} = 5.14K\Omega \quad (5)$$

Part e

As seen in the lecture, this can be calculated in the following manner

$$t_{pLH,best} = 0.69 * 5.14k * 100f = 355ps \quad (6)$$

$$t_{pHL,best} = 0.69 * 6k * 100f = 414ps \quad (7)$$

Question 2

Part a


This circuit performs the function of a NAND gate. The PASS transistor network performs AND then an inverter by M1 and M2.

Part b

When A=B=1, the pass transistor would pass up to $V_{DD} - V_{th(NMOS)}$ to the X^{nth} node. This results in M1 not completely turning off which leads to static power dissipation as both M1 and M2 are on.

Part c

This can be done in the following way:

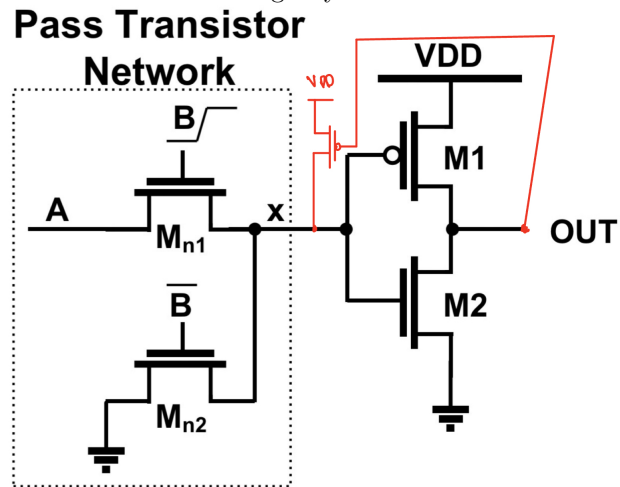

One should note that the transistor should be small enough to pull the node X to GND when B is 0

Part d

This can be done in the following way:

