

Assigment 2

Muthya Narayanachary Akhil

January 29, 2024

Question 1

Part a

As stated in the question, we are required to calculate C_{wire} , which can be expressed by the following equation:

$$C_{wire} = C_{pp} + C_{fringe} \quad (1)$$

Calculating parallel plate capacitance

Based on the lecture notes, this can be calculated in the following way:

$$C_{pp} = \frac{38 * 10^{-18}}{1 * 10^{-12}} * 250 * 10^{-6} * 0.4 * 10^{-6} = 3800 * 10^{-18} F = 3800 aF \quad (2)$$

Calculating fringing capacitance

This can be found in the following way:

$$C_{fringe} = \frac{13 * 10^{-18}}{10^{-6}} * 250 * 10^{-6} = 3250 * 10^{-18} = 3250 aF \quad (3)$$

Since fringe capacitance needs to include for both the side walls, the value needs to be doubled, that is:

$$C_{fringe} = 3250 * 2 = 6500 aF \quad (4)$$

Calculating the capacitance of the wire

Based on (2) and (4), we can determine the capacitance of the wire in the following way:

$$C_{wire} = C_{pp} + C_{fringe} = 3800 + 6500 = 10300 aF = 10.3 fF \quad (5)$$

Part b

The goal is to calculate the R_{wire} , given that the sheet metal resistance (R_0) is $0.08 \frac{\Omega}{sq}$. The width is given to be $0.4\mu m$, hence the goal is to fit as many squares of this size into the available length. This can be done in the following way:

$$R_{wire} = 0.08 * \frac{250 * 10^{-6}}{0.4 * 10^{-6}} = 50\Omega \quad (6)$$

Question 2

Part a

We are given that the current flowing through the wire is 4mA. Hence the IR drop can be given by:

$$IR_{drop} = 4 * 10^{-3} * 50 = 0.2V \quad (7)$$

Part b

We are given that the voltage source has an output impedance of 50Ω , and required to calculate the propagation delay (t_p). Based off the lecture notes, we are aware the t_p is a function of resistance when on R_{on} and the load capacitance C_L .

$$t_p = f(R_{on} \cdot C_L) = 0.69 * R_{on} * C_L \quad (8)$$

Since there is an impedance from the voltage source, R_{on} can be calculated to be:

$$R_{on} = R_{wire} + Z_{source} = 50 + 50 = 100\Omega \quad (9)$$

Based on (5) and (9) we can compute the t_p to be the following:

$$t_p = 100 * 10.3 * 10^{-15} = 7.107 * 10^{-13} = 71.07ps \quad (10)$$

Question 3


Part a

When $V_{in} = 0V$

For the NMOS inverter shown above, when V_{in} is 0V, the steady state V_{out} is 1V. This is because when V_{in} is 0V, there is no current at the gate, which doesn't lead to any holes appearing at the gate. This means that there is no channel formed to facilitate electron flow, and hence the NMOS is turned off. In short, this is because $V_{GS} < V_{TH}$ or the gate voltage is lesser than the threshold voltage. This means that the V_{DD} supply is used to charge the capacitor C_L , which would have the supply voltage across its terminals once it has been fully charged (ie at steady state).

When $V_{in} = 1V$

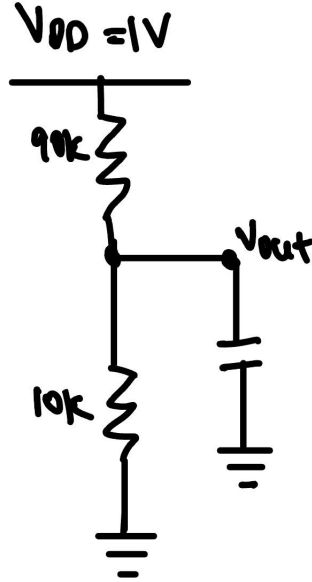However, when V_{in} is 1V, we can notice that the gate voltage is greater than the threshold voltage and the NMOS is turned on. When the NMOS can usually be considered to be a switch with a resistor. In this case the switch is turned on with a resistance of $10k\Omega$. This changes the nature of the circuit to be something like this:



We can now use Ohms law for parallel circuits to calculate V_{out} in the following manner:

$$V_{out} = V_{in} * \frac{10k\Omega}{10k\Omega + 90k\Omega} = \frac{10}{100} = 0.1V \quad (11)$$

Part b

When $V_{in} = 0V$

When $V_{in} = 0V$, this means that the NMOS is turned off as V_{GS} for the NMOS is less than the threshold voltage (V_{THN}). However, in the case of the PMOS, this means that the gate voltage is negative in terms of the supply voltage. This means that electrons accumulate on the gate, which leads to holes creating a channel for current to flow from the source to the drain. This ends up charging C_L , which ends up leading to $V_{out} = 1V$.

When $V_{in} = 1V$

When $V_{in} = 1V$, this means that the PMOS is turned off, as there is not enough potential difference to create a channel of holes. However the PMOS is turned

off as $V_{GS} > V_{THN}$. This leads to the current flowing from the drain to the source, and the capacitor is discharged, leading to the $V_{out} = 0V$.